
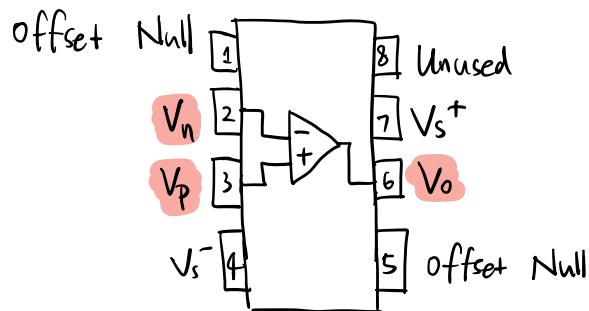


Chapter 3 : Algebraic Operations

Basic Knowledges.

1. Physical Illustration:

Diagram :

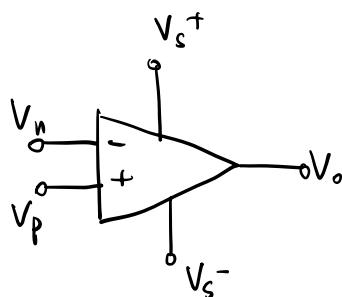

Important Terminals


$\left\{ \begin{array}{l} \text{Input: } V_n, V_p \\ \text{Output: } V_o \\ \text{power: } V_s^-, V_s^+ \end{array} \right.$

2. Open loop Connection

$$\Delta \text{gain } K \Rightarrow V_o = K(V_p - V_n) \text{ and } |V_o| \leq V_s^+$$

Saturation

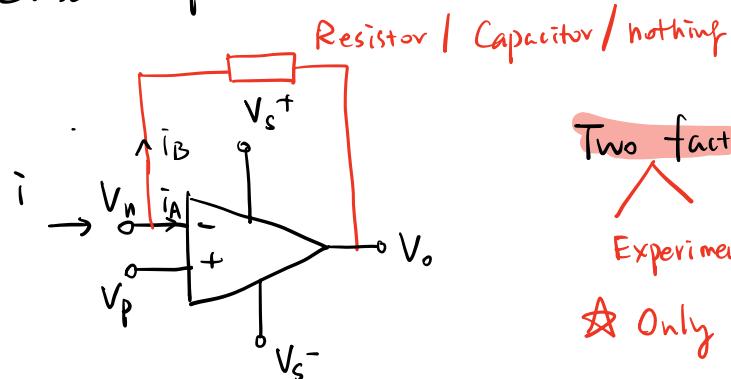3. Closed loop Connection (Feedback Configuration)



Two facts:

Experimental

★ Only exist in the feedback configuration


$$\left\{ \begin{array}{l} \bar{i}_A \approx 0 \quad \frac{1}{T_{\text{loop}}} i \\ V_n \approx V_p \end{array} \right.$$

$$\bar{i} = \bar{i}_A + \bar{i}_B \text{ and } \bar{i}_A = 0$$

$$\frac{V_n - V_o}{R} = \bar{i}_B \Rightarrow V_o = V_n - \bar{i}_B R$$


4. Basic circuits

① Buffering / Cascading

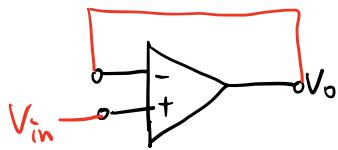


$$V_{in} = V_o$$

It seems like a direct wire connection.

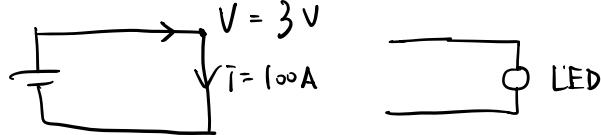


② Gain and Inverting

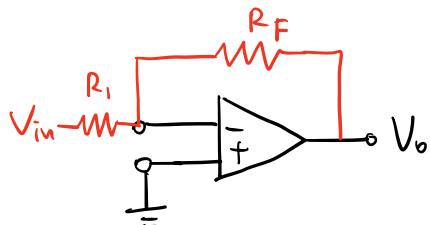

$$\frac{0 - V_o}{R_F} = \frac{V_{in}}{R_1} \Rightarrow V_o = - \frac{R_F}{R_1} V_{in}$$

↓ invert ↓ gain

③ Addition

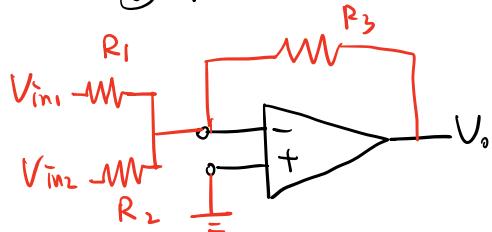

$$\frac{V_{in1} - 0}{R_1} + \frac{V_{in2} - 0}{R_2} = \frac{0 - V_o}{R_3}$$

$$\Rightarrow V_o = - \left(\frac{R_3}{R_1} V_{in1} + \frac{R_3}{R_2} V_{in2} \right)$$


If $R_1 = R_2 = R$

$$\Rightarrow V_o = - \frac{R_3}{R} \underbrace{\left(V_{in1} + V_{in2} \right)}_{\text{Addition}}$$

If $R_1 = R_2 = R_3 = R$

$$\Rightarrow V_o = - (V_{in1} + V_{in2})$$

④ Subtraction

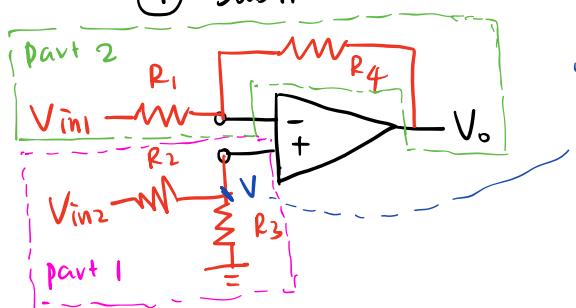

Denote the voltage V

$$\text{part 1: } \frac{V_{in2} - V}{R_2} = \frac{V}{R_3}$$

$$\Rightarrow \frac{V_{in2}}{R_2} = \left(\frac{1}{R_2} + \frac{1}{R_3} \right) V$$

$$\Rightarrow V = \frac{R_2 R_3}{R_2 + R_3} \cdot \frac{V_{in2}}{R_2} = \frac{R_3}{R_2 + R_3} V_{in2}$$


$$\text{part 2: } \frac{V_{in1} - V}{R_1} = \frac{V - V_o}{R_4}$$

$$\Rightarrow V_o = \left(\frac{R_4}{R_1} + 1 \right) V - \frac{R_4}{R_1} V_{in1} = \left(\frac{R_4}{R_1} + 1 \right) \frac{R_3}{R_2 + R_3} V_{in2} - \frac{R_4}{R_1} V_{in1} \quad \text{if } R_1 = R_2 = R_3 = R_4 = R$$


$$\text{Sub. } V \quad \Rightarrow V_o = \left(\frac{R_4}{R_1} + 1 \right) \frac{R_3}{R_2 + R_3} V_{in2} - \frac{R_4}{R_1} V_{in1} = - (V_{in1} - V_{in2})$$

Experiments Steps.

- ① Set up the power source

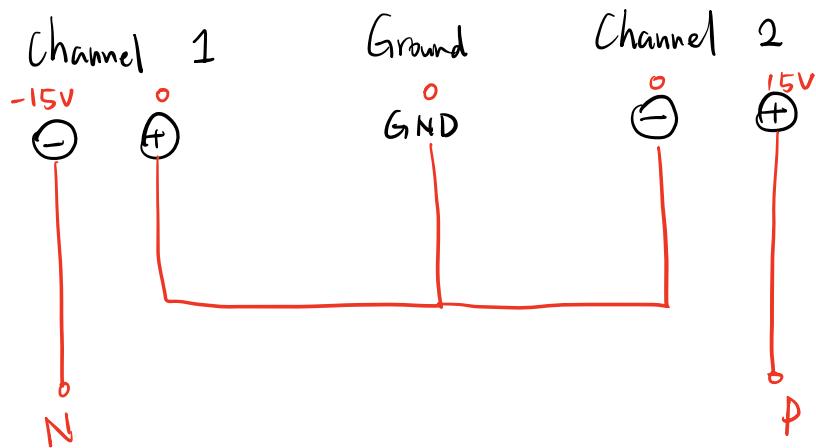


- ② A. To buffer +15V

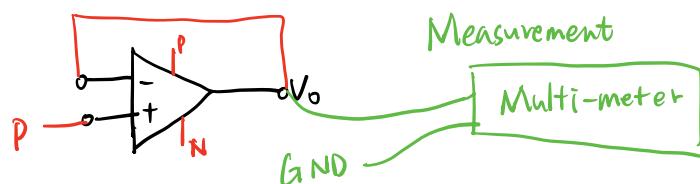


$$V_o = P$$


- B. To step down from +15V

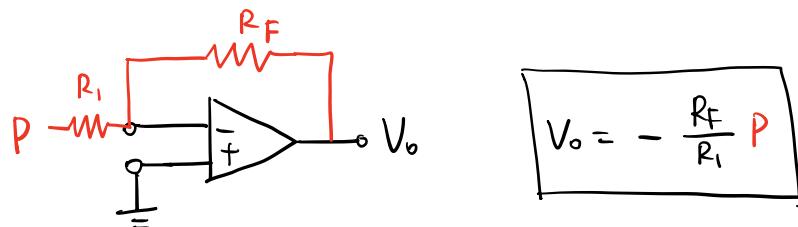


- C. To sum the A and B outputs

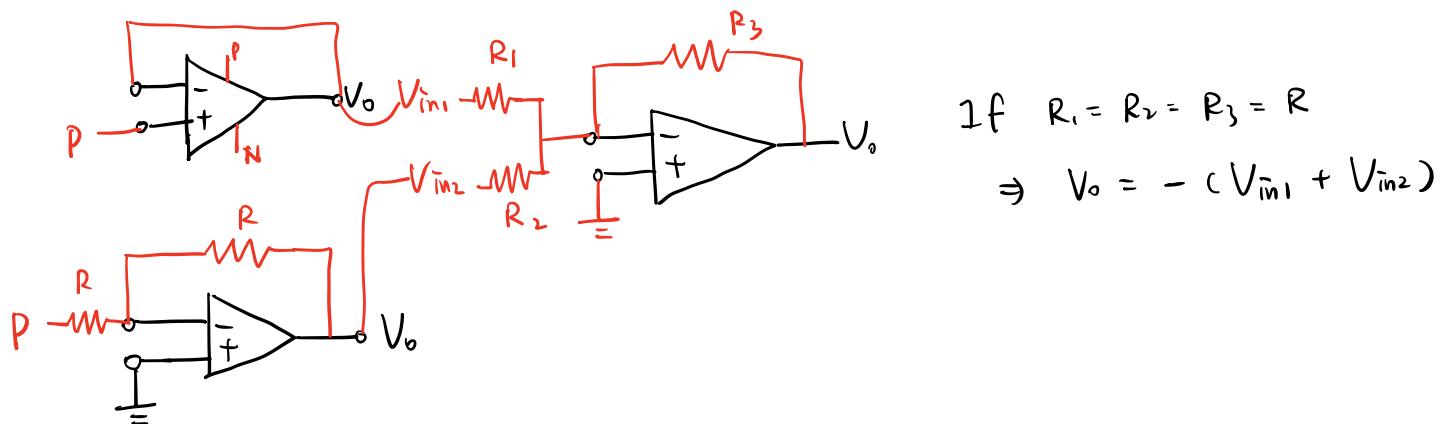

D. To invert the B output

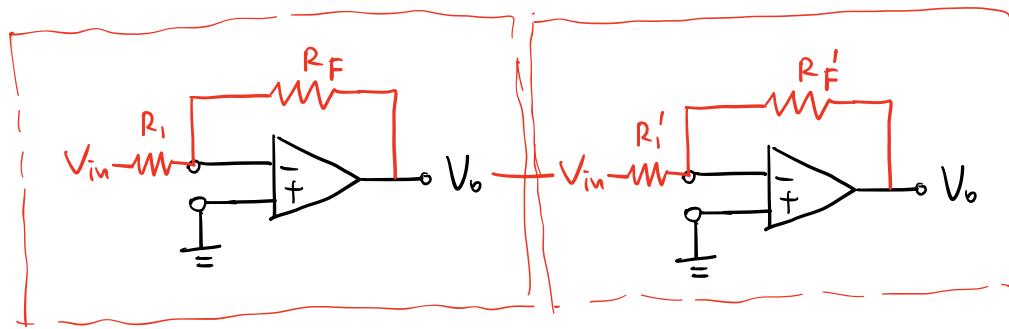

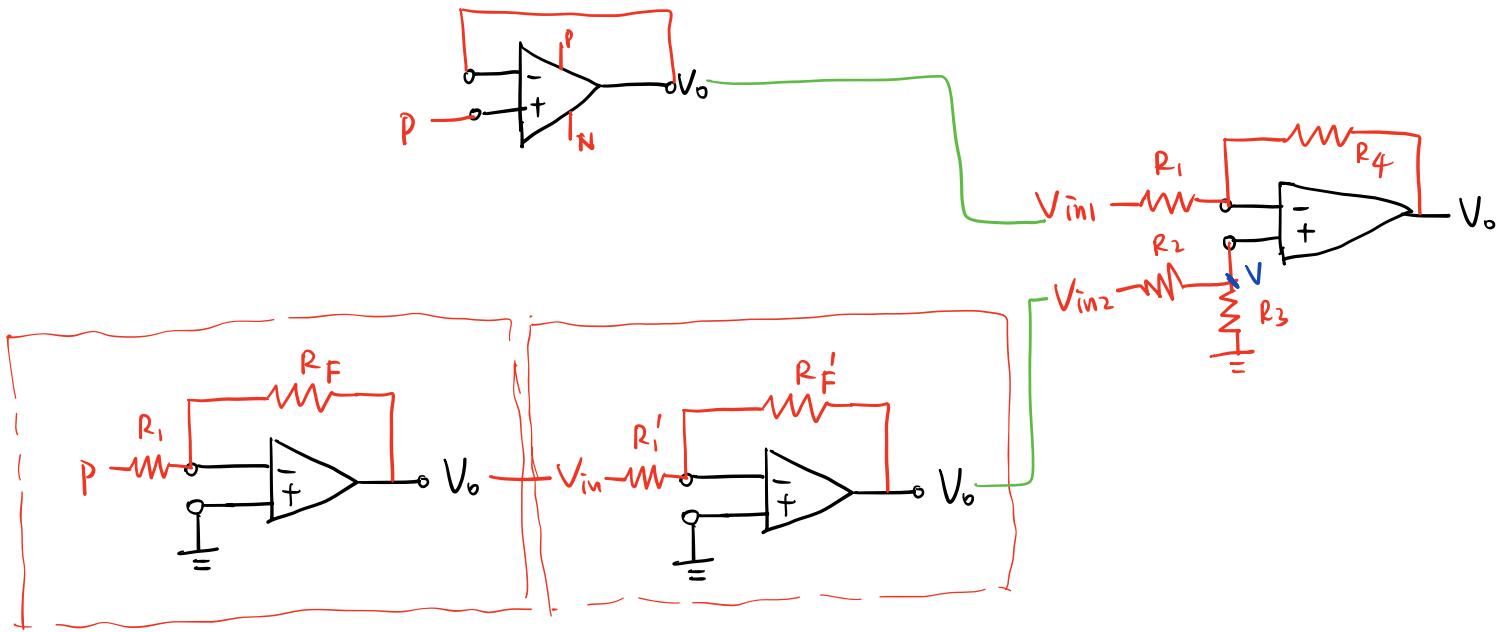E. To subtract the D output from the A output ($A - D$)



F. To get an output of 3V from the +15V input

Hints: use the parallel or series of resistors to create an "equivalent resistor" with new resistance value.